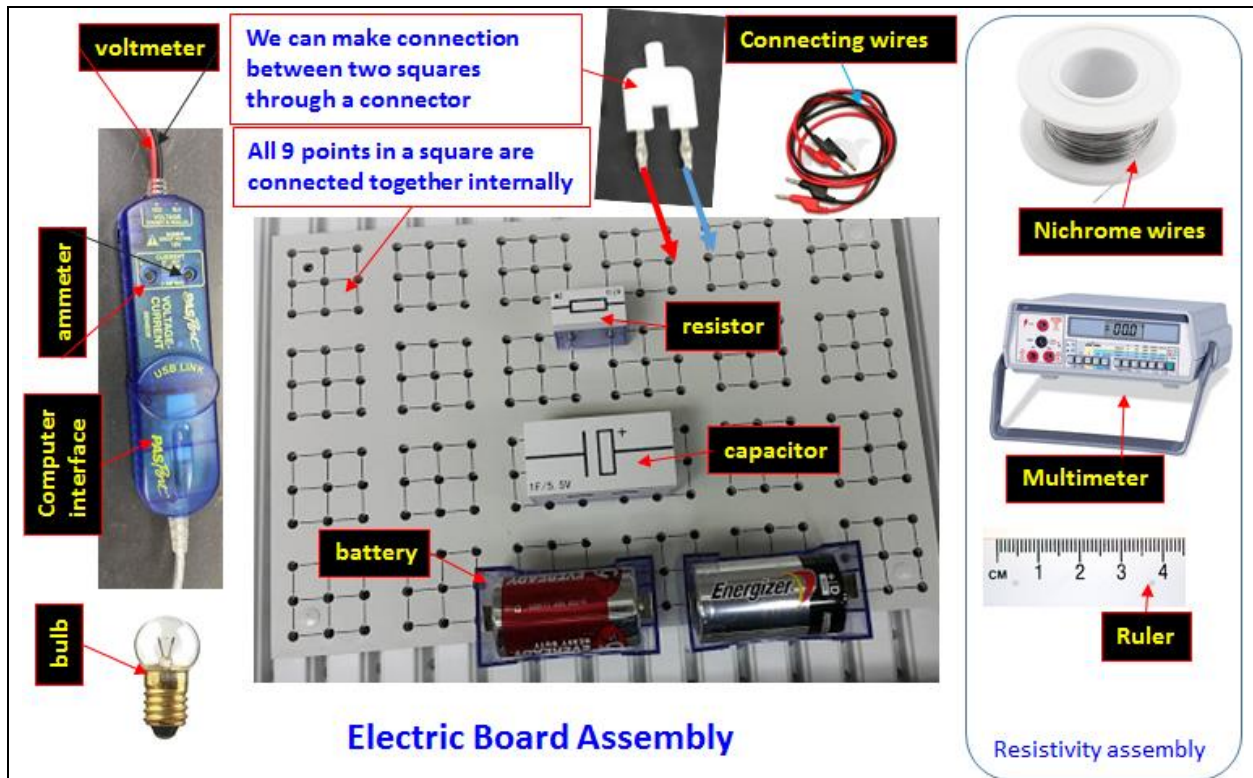


Capacitance

Objectives

- To learn the charging and discharging properties of a capacitor
- To learn about the series combination of capacitors
- To learn about the parallel combination of capacitors

Apparatus Assembly



Introduction

Capacitance

A capacitor is a device that is used to store charge and its capacity to store charge is called capacitance. Mathematically, the capacitance C , can be written as:

$$C = \frac{q}{V} \quad (1)$$

Where V is the applied potential difference and q is the quantity of the charge stored in the capacitor.

Charging of Capacitor

When an uncharged capacitor of capacitance C is connected to a battery of emf V_0 through a resistor R its voltage V increases with time and their relationship is given by the equation (2).

$$V = V_0 - V_0 e^{-t/\tau} \quad (2)$$

Where, $\tau = RC$ is the time constant, defined as the capacitor's time to charge (discharge) by 63.2%.

Discharging of capacitor

When a fully charged capacitor with initial voltage V_0 is connected in a circuit through a resistor its voltage will decrease in time according to equation (3).

$$V = V_0 e^{-t/\tau} \quad (3)$$

The process is called the discharging of the capacitor.

The current in the discharging circuit decreases in a similar manner as in the charging circuit.

Whether the process is charging or discharging, the current will exponentially increase from $t = 0$. The relationship is provided in equation (4).

$$I = I_0 e^{-t/\tau} \quad (4)$$

Parallel combination of capacitors

When n numbers of capacitors are connected in parallel each capacitor has the same amount of charge. The equivalent capacitance C_p of parallel combination can be written as:

$$C_p = C_1 + C_2 + \dots + C_n$$

If there are only two resistors in parallel combination as shown in Fig.,

$$C_p = C_1 + C_2. \quad (5)$$

Series combination of capacitors

When n -number of capacitors are connected in series they share the same potential difference. The equivalent capacitance C_s for series combination is given by the following formula:

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$

If there are only two resistors connected in series as shown in Figure,

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$C_s = \frac{C_1 C_2}{C_1 + C_2} \quad (6)$$

Part 1: Finding

In this exercise you will learn to connect the charging and discharging circuits of capacitors from the circuit diagram. Then you will find the actual value of the capacitors from charging and discharging curves.

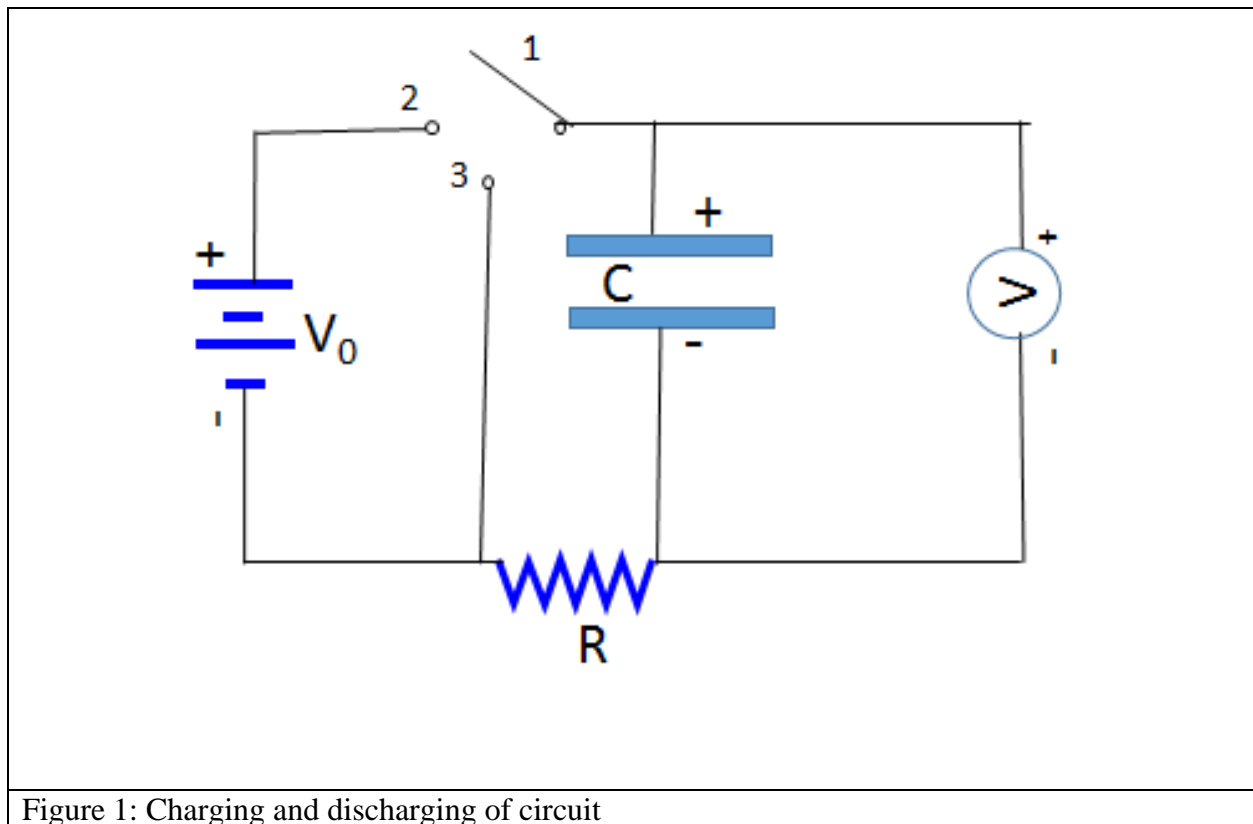


Figure 1: Charging and discharging of circuit

1. Take a connection board and identify the items in the circuit diagram. A voltmeter and ammeter are built into the Pasco I-V sensor. C is a capacitor, R is a resistor, and V_0 is the voltage of the battery.
2. Make sure you are provided with two capacitors of different values, two resistors of different values, a Pasco-voltage sensor, a power supply and wires.
3. Take a bigger valued capacitor and name it as C_1 . Read out the voltage and capacitance of the capacitor. **Never exceed the voltage limit written in the capacitor. If you ever exceed you will damage the capacitor.**
4. A resistor of resistance R is provided to you. If it is not provided then you can use the external voltmeter.
5. Multiply the values of R and C_1 . Ensure the units of R and C are Ohms and Farad respectively. The result is called time constant and it can help you estimate the

discharging time. 63.4% of the capacitor voltages discharges during $\tau = R \times C$ **This value has to be a few seconds that can be comprehensible.** For example: if the capacitor is $1000 \mu F$, the resistance is 10Ω , then, $\tau = 10 \times 1000 \times 10^{-6} = 10^{-2} s$. It is a flash of second and such time cannot be comprehensible. But if the resistance is $10 k\Omega$, $\tau = 10 \times 1000 \times 1000 \times 10^{-6} = 10 s$. Such time can be comprehensible. (Note that the sensor voltmeter also has a resistance. It is about a million Ohm. Such a high resistance in parallel does not contribute much. So, you can ignore its effect)

6. Connect the circuit diagram according to figure1 using C1 and R in the circuit.
7. Make sure the positive side of the capacitor as well as of the voltmeter are connected to the positive side of the battery.
8. Make sure points 1, 2, and 3 are open. They should not be connected to each other. A cable with a banana connector can be used as a two-way connector.
9. Don't turn on the power supply yet.
10. Connect the I-V sensors to the computer through the interface.
11. Open data studio/new experiment/graph
12. Set Voltage v/s time graph.
13. Turn on the power supply. Set the power supply voltage V_0 at any value between 5 to 10 V. Check on the capacitor label and make sure the labeled voltage on capacitor is greater than V_0 .
- 14. Have your instructor verify your connection.**
15. Start data studio. The voltage-time graph should read zero. If not, discharge the capacitor by directly connecting the two terminals of the capacitor.
16. Connect points 1 and 2 in the circuit diagram so that the capacitor will be connected to the battery and gets charged.
17. Once the voltage reading in the data studio saturates to V_0 disconnect points 1 and 2 and connect 1 and 3. The voltage goes down and you get a discharged curve. Stop the software once the voltage turns to a flat line (almost zero V). This means the capacitor is completely discharged. The charging and discharging curve would look like **Figure 2**.

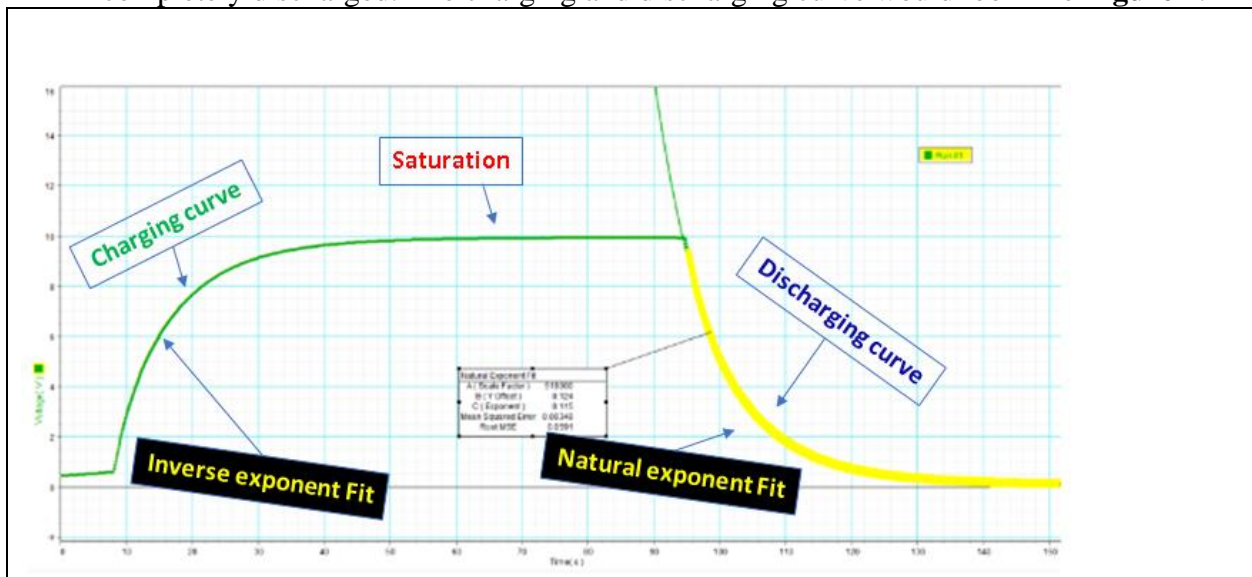


Figure 2: Charging and discharging curves taken by Data Studio

18. Find the exponent of the curve by the exponential curve fitting. (**Inverse Exponent Fit** for charging curve and **Natural Exponent Fit** for discharging curve.)
19. The charging and discharging equations infer that the absolute value of exponent, $E = \frac{1}{RC_1}$. Find the value of C_1 from the average value of exponents and fill in **Table 1**.
20. Calculate the theoretical value of voltage V_τ at time $\tau = RC$ (63.2% of maximum voltage). Use the axes tool in the data studio to find the experimental value of V_τ and fill in **Table 1**.
21. Measure the experimental value of V_τ using coordinate tool and compare it with the theoretical value. (**Find the voltage difference between time $t = 0$ to $t = RC$ from either charging or discharging curve. Make sure you are taking $t = 0$ while charging or discharging starts, not from when you run the time**)

Capacitor	R(Ω)	E _{ch}	E _{dch}	E _{av}	$C = \frac{1}{RE_{av}}$ (μF)	C _{th} (μF)	C %_error	V τ _{ex} (V)	V τ _{th} (V)	V τ %_error
C1						x	x			
C2						x	x			
Cs										
CP										

Table 1: Data analysis summery

E_{ch} = Absolute value of exponent from the charging curve

E_{dch} = Absolute value of exponent from the charging curve

E_{av} = average value of exponent

C_{th} = theoretical (expected value of C)

V τ _{ex} = experimental value of voltage while charging (discharging) happens from start time to $t = RC$.

V τ _{th} = 0.632 V₀.

22. You can get the value of exponent from current equation as well. However, the current is too small to be detected by our sensors.

Part 2: Finding the capacitance of second capacitor: C₂

1. Replace capacitor C_1 with the second capacitor C_2 in the circuit. Delete all runs on Data studio.
2. Repeat steps 15 to 21 and fill in the result in **Table 1**.

Part 3: Investigating series combination of capacitors.

1. Connect two capacitors in series as shown in **Figure 3**.
2. Delete all runs on Data studio.
3. Repeat steps 15 to 21 and fill in the result in **Table 1**.
4. Find expected value from the theory equation (6).

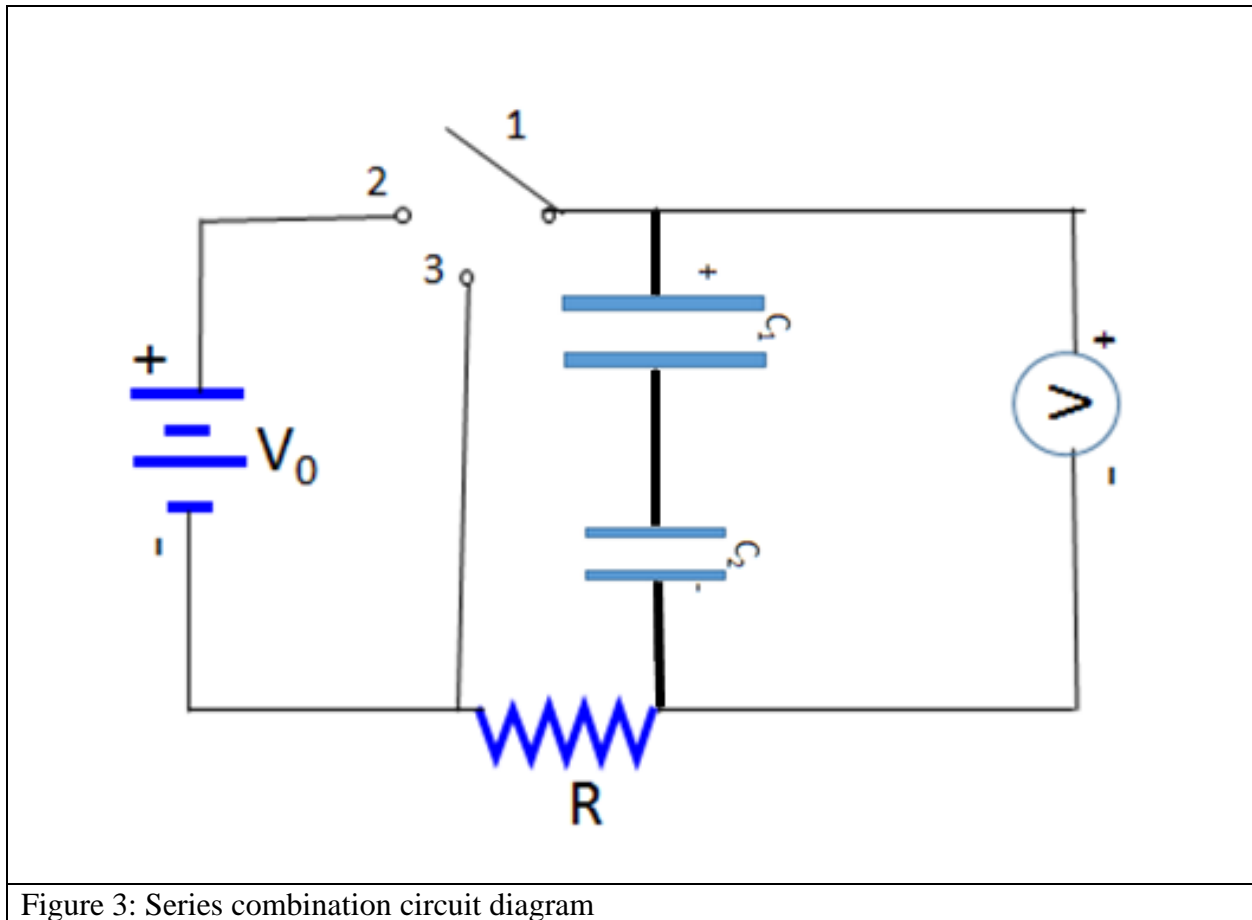


Figure 3: Series combination circuit diagram

Part 4: Investigating the parallel combination of capacitors.

1. Connect two capacitors in parallel as shown in **Figure 4**.
2. Delete all runs on Data studio.
3. Repeat steps 15 to 21 and fill in the result in **Table1**.
4. Find expected value from the theory equation (5).

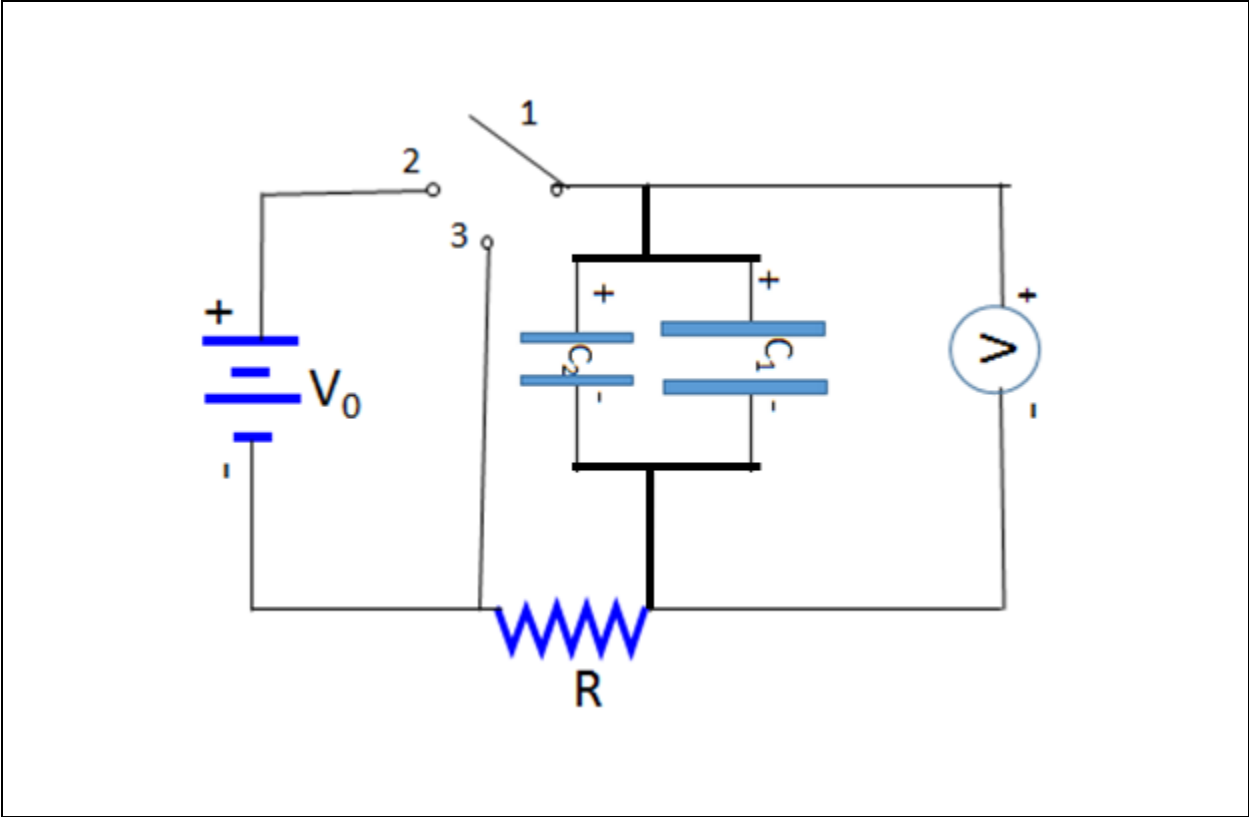


Figure 4: Parallel combination circuit diagram